

Presentation Topic

AADE

Faculty Name-AHER V.N.
Faculty official (VIIT) mail Id
Department of E& TC Engineering



BRACT'S, Vishwakarma Institute of Information Technology, Pune-48

(An Autonomous Institute affiliated to Savitribai Phule Pune University)
(NBA and NAAC accredited, ISO 9001:2015 certified)

Analog and Digital Electronics

**(Second Year BTech IT)
(2020-21)**

(Faculty: AHER V.N.)

Courtesy: R. P. Jain
(Modern Digital Electronics)

Combinational Logic

(UNIT- 2)

Combinational Logic

Design of Combinational Logic:

Code converter - BCD, Excess-3, Gray code, Binary Code.

Half- Adder, Full Adder, Half Subtractor, Full Subtractor,

Binary Adder (IC 7483), BCD adder, Look ahead carry generator,

Multiplexers (MUX): MUX (IC 74153, 74151), MUX tree,

Demultiplexers (DEMUX)- Decoder. (IC 74138, IC 74154).


DMUX Tree, Implementation of SOP and POS using MUX,

DMUX, Comparators, Parity generators and Checker, One bit,


Two bit , 4-bit Magnitude Comparator

Two Types of Networks

 Combinational: Output values depend only on *present* input values.



 Sequential: Output values depends on present *and* past input values.
i.e. A *sequence* of I/P values must be specified to define the O/P.



Why Digital ??

- Why digital?**
- greater accuracy & reliability
 - more versatile & cheaper
 - more comprehensive theory and algorithms
 - availability of CAD tools
 - optimized device processes

Digital circuits used in:

Digital Computers	Data Processing
Electronic Calculators	Instrumentation
Control Devices	etc.
Communication Equipment	Telephone Networks, Cell Phones, CD Players, Medical Equipment, Modern TV sets, Modern Radios, etc.

Analog Systems

Advantages

- most physical phenomena of interest are analog
- transducers are simple
- potentially high precision

Disadvantages

- behaviour of analog components is subject to drift distortion, noise, offsets, etc.
- errors in analog signals accumulate during processing, transmission, and storage
- only relatively simple signal processing is practical for most applications

Digital Circuits

Advantages

- the strength of digital signals is easily restored
- signal accuracy degrades very little during processing, transmission and storage
- digital components are cheap, reliable and low-power
- digital signal processing can be highly sophisticated using special-purpose hardware or programmable digital computers

Disadvantages

- signal precision is limited by the number of bits used to encode each sample
- analog-to-digital converters and digital-to-analog converters are required to interface a digital system with real-world analog signals

Combinational Logic

Codes Converter:

- **BCD**
- **Excess-3**
- **Gray Code**
- **Binary Code Conversion**

Definations

Natural BCD Code: Decimal digits 0 through 9 are represented by their natural binary equivalents using 4 bits.

Excess 3 code: Another BCD code in 4 bit binary code. The decimal digit is obtained by adding 3 to the natural BCD code.

Gray code: It is a code in which each gray code number differs from the preceding & succeeding number by a single bit.

Construction of Gray Code:

1. A 1 bit gray code has two code words 0 and 1 representing decimal numbers 0 & 1 respectively.
2. An n-bit ($n \geq 2$) gray code will have first 2^{n-1} gray codes of (n-1) bits written in order with a leading 0 appended.
3. The last 2^{n-1} gray codes will be equal to the gray code words of an (n-1) bit gray code written in reverse order with a leading 1 appended.

Continue....

1. 1 bit gray code

Decimal number

Gray Code

0

0

1

1

2. 2 bit gray code

Decimal number

Gray Code

0

0

0

1

0

1

2

1

1

3

1

0

3. 3 bit Gray Code

Decimal number

Gray Code

0

0

0

0

1

0

0

1

2

0

1

1

3

0

1

0

4

1

1

0

5

1

1

1

6

1

0

1

Arithmetic Operations

- **Binary Addition**
- **Subtraction**
- **Multiplication**
- **Division**
- **BCD Addition**

Binary Adders

- ◆ *Half-adder*: the circuit accepts two inputs, A and B , and generates two outputs, SUM and CARRY according to the table
- ◆ Half adder truth table

<i>Inputs</i>		<i>Outputs</i>	
<i>A</i>	<i>B</i>	SUM	CARRY
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1


Binary Adders

- ◆ The Boolean expression for SUM and CARRY:

$$\text{SUM} = A'B + AB'$$

$$\text{CARRY} = AB$$

- ◆ Half adder circuit

 

Binary Adders

- ◆ *Full adder*: adds two binary digits A and B together with a 'carry-in' from a previous addition. A full adder has three inputs, A , B and 'CARRY-IN' (abbreviated here to C_{in}), and two outputs, SUM and 'CARRY OUT' (abbreviated to C_{out})
- ◆ Full adder circuit

<i>Inputs</i>			<i>Outputs</i>	
A	B	C_{in}	SUM	C_{out}
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1


Binary Adders

- ◆ The Boolean expression for SUM and C_{out} :

$$SUM = A'B'C_{in} + A'BC'_{in} + AB'C'_{in} + ABC_{in}$$

$$C_{out} = \underline{A'BC_{in}} + AB'C_{in} + ABC'_{in} + \underline{ABC_{in}}$$

- ◆ Full adder circuit

 

Binary Adders


- ◆ A full adder can also be formed from two half adders

$$\begin{aligned}
 \text{SUM} &= \bar{A}\bar{B}C_{\text{in}} + \bar{A}B\bar{C}_{\text{in}} + A\bar{B}\bar{C}_{\text{in}} + ABC_{\text{in}} \\
 &= C_{\text{in}}(\bar{A}\bar{B} + AB) + \bar{C}_{\text{in}}(\bar{A}B + A\bar{B}) \\
 &= C_{\text{in}}(\overline{\bar{A}B + A\bar{B}}) + \bar{C}_{\text{in}}(\bar{A}B + A\bar{B}) \\
 &= C_{\text{in}}(\overline{A \oplus B}) + \bar{C}_{\text{in}}(A \oplus B) \\
 &= C_{\text{in}} \oplus (A \oplus B)
 \end{aligned}$$

$$\begin{aligned}
 C_{\text{out}} &= \bar{A}BC_{\text{in}} + A\bar{B}C_{\text{in}} + AB\bar{C}_{\text{in}} + ABC_{\text{in}} \\
 &= C_{\text{in}}(\bar{A}B + A\bar{B}) + AB(\bar{C}_{\text{in}} + C_{\text{in}}) \\
 &= C_{\text{in}}(\bar{A}B + A\bar{B}) + AB \\
 &= C_{\text{in}}(A \oplus B) + AB
 \end{aligned}$$

Binary Adders


◆ Implementation of a full adder

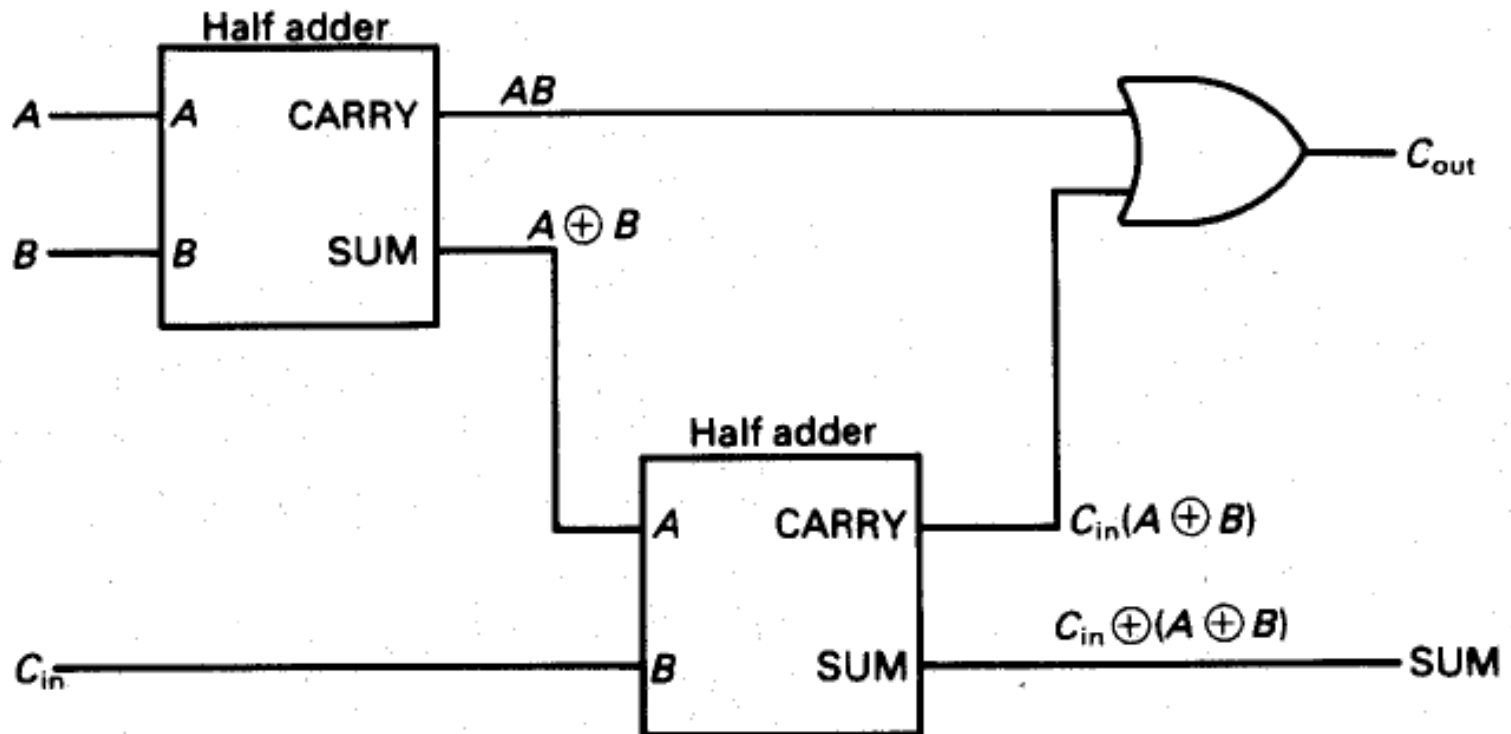

Binary Parallel Adders

- ***Parallel adder*** : a digital circuit that produces the arithmetic sum of two binary numbers in parallel. It consists of full-adders connected in a chain, with the output carry from each full-adder connected to the input carry of the next fulladder in the chain.
- The figure shows the interconnection of four full-adder (FA) circuits to provide a 4-bit binary parallel adder

Binary Parallel Adders

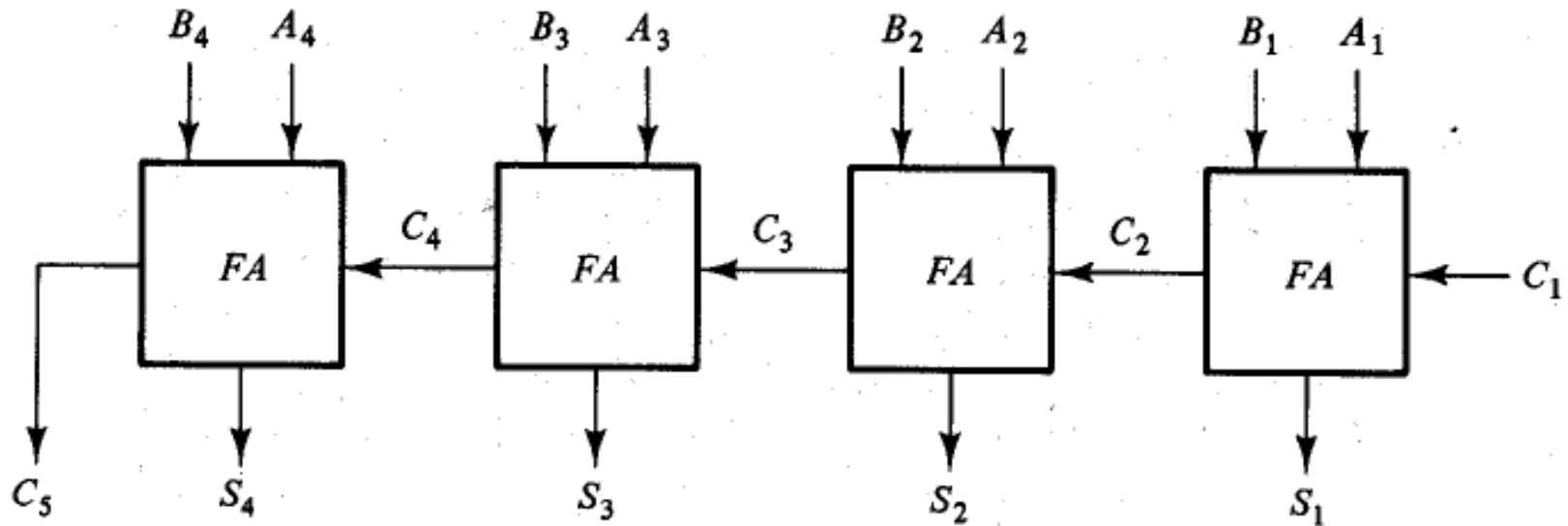


(a) 4-bit parallel adder

- ◆ Carry propagation: The longest propagation delay time in a parallel adder is the time it takes the carry to propagate through the full adders

Binary Parallel Adders

 - ◆ The carry propagation time is a limiting factor on the speed with which two numbers are added in parallel
 - Employ faster gates with reduced delays
 - Increase the equipment complexity to reduce the delay time, for example, *look-ahead* carry
- ◆ Consider the circuit of the full-adder:



Binary Parallel Adders

- ◆ If we define two new binary variables:

$$P_i = A_i \oplus B_i$$

$$G_i = A_i B_i$$

- ◆ G_i is called a *carry generate* and it produces an output carry when both A_i and B_i are one, regardless of the input carry
- ◆ P_i is called a *carry propagate* because it is the term associated with the propagation of the carry from C_i to C_{i+1}

Binary Parallel Adders

- ◆ The output sum and carry can be expressed as

$$S_i = P_i \oplus C_i$$

$$C_{i+1} = G_i + P_i C_i$$

- ◆ Carry output of each stage:

$$C_2 = G_1 + P_1 C_1$$

$$C_3 = G_2 + P_2 C_2 = G_2 + P_2(G_1 + P_1 C_1) = G_2 + P_2 G_1 + P_2 P_1 C_1$$

$$C_4 = G_3 + P_3 C_3 = G_3 + P_3 G_2 + P_3 P_2 G_1 + P_3 P_2 P_1 C_1$$

Binary Adders

- **Half Subtractor:** A logic circuit for the subtraction of B (Subtrahend) from A (minuend) where A and B are 1-bit numbers is referred to as a half-subtractor. A and B are two inputs and D (difference) and C (borrow) are the two outputs.

Truth Table:

Inputs		Outputs	
A	B	D	C
0	0	0	0
0	1	1	1
1	0	1	0
1	1	0	0

From the truth table the logical expression for D & C is:

$$D = \bar{A}B + A\bar{B} = A \oplus B \quad \& \quad C = \bar{A}B$$

Binary Adders

- **Full Subtractor:** Like a full-adder we require a full-subtractor circuit for performing multibit subtraction wherein a borrow from the previous bit position may be present as input.
- It will have three inputs, A (minuend), B (subtrahend), C (borrow from the previous stage) and two outputs, D (difference) and C (borrow).
- The truth table is:

Inputs			Outputs	
A_n	B_n	C_{n-1}	D_n	C_n
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	0	1
1	0	0	1	0
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1

Adders And Their Use As Subtractors

- We can perform both addition & subtraction using only adders because the problem of subtraction becomes that of addition when we use 1's & 2's complement representation of negative numbers.



Simplify Boolean Expressions



$$\begin{aligned}C_{out} &= \overline{A} B C_{in} + A \overline{B} C_{in} + A B \overline{C_{in}} + A B C_{in} \\&= \overline{A} B C_{in} + A B C_{in} + A \overline{B} C_{in} + A B C_{in} + A B \overline{C_{in}} + A B C_{in} \\&= (\overline{A} + A) B C_{in} + A (\overline{B} + B) C_{in} + A B (\overline{C_{in}} + C_{in}) \\&= B C_{in} + A C_{in} + A B \\&= (B + A) C_{in} + A B\end{aligned}$$

$$\begin{aligned}S &= \overline{A} \overline{B} C_{in} + \overline{A} B \overline{C_{in}} + A \overline{B} \overline{C_{in}} + A B C_{in} \\&= (\overline{A} \overline{B} + A B) C_{in} + (\overline{A} B + A \overline{B}) \overline{C_{in}} \\&= \overline{(A \oplus B)} C_{in} + (A \oplus B) \overline{C_{in}} \\&= A \oplus B \oplus C_{in}\end{aligned}$$




Simple Example: One Bit Adder



■ 1-bit binary adder

 - inputs: A, B, Carry-in
- outputs: Sum, Carry-out



A	B	Cin	S	Cout
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

Sum-of-Products Canonical Form

$$S = \bar{A} \bar{B} C_{in} + \bar{A} B \bar{C}_{in} + A \bar{B} \bar{C}_{in} + A B C_{in}$$

$$C_{out} = \bar{A} B C_{in} + A \bar{B} C_{in} + A B \bar{C}_{in} + A B C_{in}$$

■ Product term (or minterm)

- ANDed product of literals – input combination for which output is true
- Each variable appears exactly once, in true or inverted form (but not both)



Sum-of-Products & Product-of-Sum



- Product term** (or minterm): ANDed product of literals – input combination for which output is true

A	B	C	minterms	
0	0	0	$\bar{A} \bar{B} \bar{C}$	m0
0	0	1	$\bar{A} \bar{B} C$	m1
0	1	0	$\bar{A} B \bar{C}$	m2
0	1	1	$\bar{A} B C$	m3
1	0	0	$A \bar{B} \bar{C}$	m4
1	0	1	$A \bar{B} C$	m5
1	1	0	$A B \bar{C}$	m6
1	1	1	$A B C$	m7

short-hand notation form in terms of 3 variables

F in canonical form:

$$F(A, B, C) = \sum m(1, 3, 5, 6, 7)$$

$$= m1 + m3 + m5 + m6 + m7$$

$$F = \bar{A} \bar{B} C + \bar{A} B C + A \bar{B} C + A B \bar{C} + A B C$$

canonical form \neq minimal form

$$F(A, B, C) = \bar{A} \bar{B} C + \bar{A} B C + A \bar{B} C + A B C + A B \bar{C}$$

$$= (\bar{A} \bar{B} + \bar{A} B + A \bar{B} + A B) C + A B \bar{C}$$

$$= ((\bar{A} + A)(\bar{B} + B)) C + A B \bar{C}$$

$$= C + A B \bar{C} = A B \bar{C} + C = A B + C$$

- Sum term** (or maxterm) - ORed sum of literals – input combination for which output is false

A	B	C	maxterms	
0	0	0	$A + B + C$	M0
0	0	1	$A + B + \bar{C}$	M1
0	1	0	$A + \bar{B} + C$	M2
0	1	1	$A + \bar{B} + \bar{C}$	M3
1	0	0	$\bar{A} + B + C$	M4
1	0	1	$\bar{A} + B + \bar{C}$	M5
1	1	0	$\bar{A} + \bar{B} + C$	M6
1	1	1	$\bar{A} + \bar{B} + \bar{C}$	M7

short-hand notation for maxterms of 3 variables

F in canonical form:

$$F(A, B, C) = \prod M(0, 2, 4)$$

$$= M0 \cdot M2 \cdot M4$$

$$= (A + B + C) (A + \bar{B} + C) (\bar{A} + B + C)$$

canonical form \neq minimal form

$$F(A, B, C) = (A + B + C) (A + \bar{B} + C) (\bar{A} + B + C)$$

$$= (A + B + C) (A + \bar{B} + C)$$

$$(A + B + C) (\bar{A} + B + C)$$

$$= (A + C) (B + C)$$



Mapping Between Forms



1. **Minterm to Maxterm conversion:**
rewrite minterm shorthand using maxterm shorthand
replace minterm indices with the indices not already used

$$\text{E.g., } F(A,B,C) = \sum m(3,4,5,6,7) = \prod M(0,1,2)$$

2. **Maxterm to Minterm conversion:**
rewrite maxterm shorthand using minterm shorthand
replace maxterm indices with the indices not already used

$$\text{E.g., } F(A,B,C) = \prod M(0,1,2) = \sum m(3,4,5,6,7)$$

3. **Minterm expansion of F to Minterm expansion of F':**
in minterm shorthand form, list the indices not already used in F

$$\begin{array}{ccc} \text{E.g., } F(A,B,C) = \sum m(3,4,5,6,7) & \longrightarrow & F'(A,B,C) = \sum m(0,1,2) \\ & \longrightarrow & = \prod M(3,4,5,6,7) \\ & & = \prod M(0,1,2) \end{array}$$

4. **Minterm expansion of F to Maxterm expansion of F':**
rewrite in Maxterm form, using the same indices as F

$$\begin{array}{ccc} \text{E.g., } F(A,B,C) = \sum m(3,4,5,6,7) & \longrightarrow & F'(A,B,C) = \prod M(3,4,5,6,7) \\ & \longrightarrow & = \sum m(0,1,2) \\ & & = \prod M(0,1,2) \end{array}$$

BCD ARITHMETIC

BCD Adder:

- 4-bit binary adder IC(7483) can be used to perform addition of BCD numbers.
- If 4-bit sum output is not a valid BCD digit, or if a carry C is generated, then decimal 6 (0110) is to be added to the sum to get the correct result.
- It can be cascaded to add numbers several digits long by connecting the carry-out of a stage to the carry-in of the next stage.

BCD Subtractor:

- 9's complement of the subtrahend is added to the minuend.
- 9's complement of a BCD number is given by nine minus that number.
- E.g. 9's complement of 7 = $9 - 7 = 2$.
- i.e. in BCD code 9's complement of 0 1 1 1 is 0 0 1 0.

BCD ARITHMETIC

BCD Addition:

- In BCD addition we have to deal with 3 different situations. Assume two 4 bit BCD numbers A & B are added. Then the 3 cases to be considered are:

Case 1: Sum is equal to or less than 9 and carry is 0.

E.g. Addition of decimal nos. 2 and 6 in BCD gives result as 8.
Thus we can say sum is in proper BCD form and requires no correction.

Case 2: Sum is greater than 9 and carry is 0.

E.g. Addition of decimal nos. 7 & 6 in BCD gives result as 13. Since sum is greater than 9, it is a invalid BCD number, with carry 0. so to correct the sum, add decimal 6 or BCD 0110 to sum to get the correct BCD sum.


Case 3: Sum is less than or equal to 9 but carry is 1.

E.g. Addition of decimal nos. 9 & 8 gives result as 17. We get sum as a valid BCD and carry =1, but the result is a incorrect BCD result. So add 6 to the sum obtained to get the correct BCD result.


Note: The addition is to be carried out as normal binary addition.

BCD ARITHMETIC

Summary of BCD Addition:

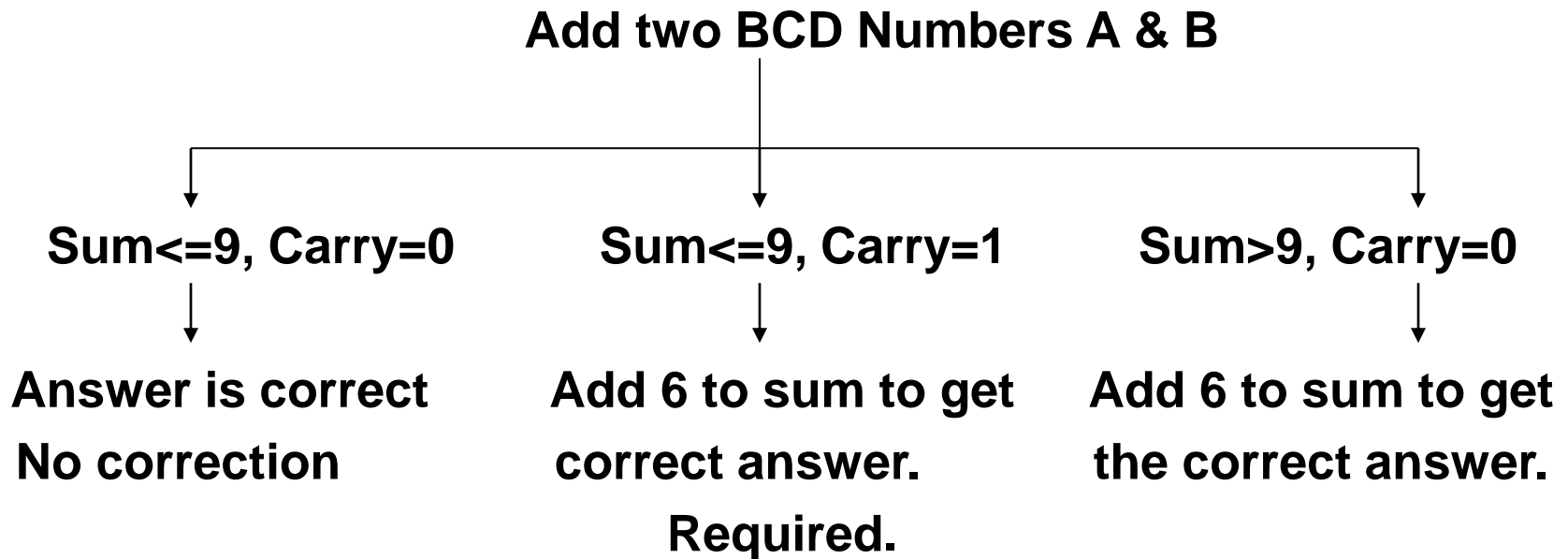

BCD ADDER

 

BCD ARITHMETIC

BCD Subtraction:

- The subtraction of 2 BCD numbers A & B can be performed using one of the two methods:

1. Nine's Complement Method:

9's complement of a BCD number is obtained by subtracting it from 9.
e.g. 9's complement of 1 is 8. It is similar to subtraction using 1's complement.

Step 1: Obtain 9's complement of number B.

Step 2: Add A and 9's complement of B.

Step 3: If a carry is generated in step 2 then add it to the sum to obtain the final result. The carry is called as end around carry.

Step 4: If carry is not produced then the result is negative hence take the 9's complement of the result.

e.g. Subtract decimal no. 3 from 7 in BCD. i.e. $9 - 3 = 6$, add 7 & 6 to get 13 add 1 which is end around carry to 3 to get result as 4.

BCD ARITHMETIC

- BCD Subtraction using 9's complement to represent negative numbers.
- E.g. Subtract 5 from 9

$$\begin{array}{rcl} 9 = & 1001 & \\ -5 = & (+)0100 & \text{(9's complement of 5 i.e. } 9-5=4\text{)} \\ & \hline & 1101 & \text{(invalid)} \\ \text{Add} & 0110 & \\ & \hline & 10011 & \\ & \text{1} & \text{Add End Around Carry (EAC)} \\ & \hline & 0100 & = +4 \end{array}$$

E.g. Subtract 1 from 8

Ans. = +7

E.g. Subtract 8 from 4

Ans. = -4

BCD ARITHMETIC

2. Ten's Complement Method:

- It is obtained by adding 1 to the 9's complement.
- 10's complement can be used to perform the BCD subtraction as:

Step 1: Obtain the 10's complement of subtrahend (number to be subtracted).

Step 2: Add the minuend to the 10's complement of subtrahend.

Step 3: Discard carry. If carry is 1 then the answer is positive and is in its true form.

Step 4: If carry is not produced then the answer is negative. So take 10's complement to get the answer.

E.g . Perform the subtraction of decimal nos. $9 - 4$ in BCD using 10's complement.

Ans. 5

BCD ARITHMETIC

Signed Magnitude BCD Numbers:

- The representation of signed decimal numbers in BCD is similar to the representation of signed numbers in binary.
- The sign of a decimal number is generally represented with four bits. The plus sign is denoted by four zeros and minus with the BCD equivalent of 9 i.e. 1001.
- E.g. Represent the numbers +52 and -52 in the signed magnitude form.

➤ + 5 2
➤ 0000 0101 0010

- 5 2
1001 0101 0010



Combinational Logic

- It involves simplification and realization using gates.
- It consists of an array of devices such as multiplexers, demultiplexers, adders, parity generators/checkers, priority encoders, decoders, comparators etc.
- Combinational logic is the general term for blocks of digital logic which contain no kind of memory
- The output of a block of combinational logic is determined solely by its inputs
- The relationship between the inputs and outputs is specified by the *truth table*
- For a logic block with n inputs, there are 2^n entries in the truth table
- Simple adders are an example of combinational logic
- So is the ALU, but this is much more complex.
- Registers are not combinational logic, since they contain memory.

Combinational logic example

- Consider a block of combinational logic with two inputs and four outputs
- Each of the four possible input combinations uniquely selects only one of the four outputs

I1	I2	Q1	Q2	Q3	Q4
0	0	1	0	0	0
0	1	0	1	0	0
1	0	0	0	1	0
1	1	0	0	0	1

- This is known as a decoder
- Used commonly in memories to select a unique memory location based on an address
- No storage capability: when the input changes, the output changes after a short propagation delay

Multiplexer

- Passes one of several data inputs to output.
- Generally 2^n data inputs and always a single data output.
- n control lines determine which input is “steered” to the output.
- Allows logical (not “tri-state” or electrical) implementation of buses.
- Buses and register transfer operations fundamental to digital system design.
- Also possible to implement arbitrary combinational logic with multiplexers.
- Universal, combinational logic element.
- Also known as “Data Selector” and “Mux”.
- In sequential operation, provides parallel to serial Conversion.

Multiplexer Advantages

- **Simplification of logic expression is not required.**
- **Minimizes the IC package count.**
- **Logic design is simplified.**
- **It can be used as a logic element in the design of combinational circuits.**
- **The standard ICs available are 2:1, 4:1, 8:1 and 16:1.**

Design Procedure:


- 1. Identify the decimal number corresponding to each minterm in the expression, & connect the input lines corresponding to these numbers to logic 1 level.**
- 2. Connect all other input lines to logic 0 level.**
- 3. Apply inputs to select inputs.**

Multiplexer Tree:

- **To achieve larger input needs there is a provision for expansion, which is designed with the help of enable/strobe inputs and multiplexers stacks or trees.**

Multiplexers

 = Multiplexors are clearly something that we need to know how to build




I1	I2	S	Q
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	1

= It is possible to write a logic equation for Q in terms of I1, I2 and S:

$$Q = (I1 \cdot \overline{S}) + (I2 \cdot S)$$

= The logic circuit follows trivially

Multiplexers from logic

 

- = Note the shorthand for NOT, this is very commonly used
- = Obviously this is only a single-bit multiplexer, it should be obvious that to multiplex two 32-bit numbers, you need 32 of these controlled by the same “select” signal
- = You should verify that this does what is intended

Two-to-One Multiplexer


$$F = \text{Select}' \cdot x_0 + \text{Select} \cdot x_1$$

$$x_1 = w_0$$

$$x_2 = w_1$$

$s \ x_1 x_2$	$f(s, x_1, x_2)$
0 0 0	0
0 0 1	0
0 1 0	1
0 1 1	1
1 0 0	0
1 0 1	1
1 1 0	0
1 1 1	1


s	f
0	w_0
1	w_1

 

(a) Graphical symbol

(b) Truth table

s	$f(s, x_1, x_2)$
0	x_1
1	x_2

 


(c) Sum-of-products circuit

 (a) Truth table (d) More compact truth-table representation

Four to One Multiplexer

- i^{th} data input ANDed with minterm m_i
- Embedded circuit generating minterms
- will become known as a decoder




(a) Graphical symbol

s_1	s_0	f
0	0	w_0
0	1	w_1
1	0	w_2
1	1	w_3

(b) Truth table

$$f = \bar{s}_1 \bar{s}_0 w_0 + \bar{s}_1 s_0 w_1 + s_1 \bar{s}_0 w_2 + s_1 s_0 w_3$$

$m_0 w_0$ $m_1 w_1$ $m_2 w_2$ $m_3 w_3$

 


(c) Circuit

Figure 6.2 A 4-to-1 multiplexer


Building Larger Multiplexers

 - 4-to-1 (4:1) Mux using 2-to-1 (2:1) Muxes
- Simple and modular
- Adds 2 levels of gate (propagation) delay




Building Larger Multiplexers

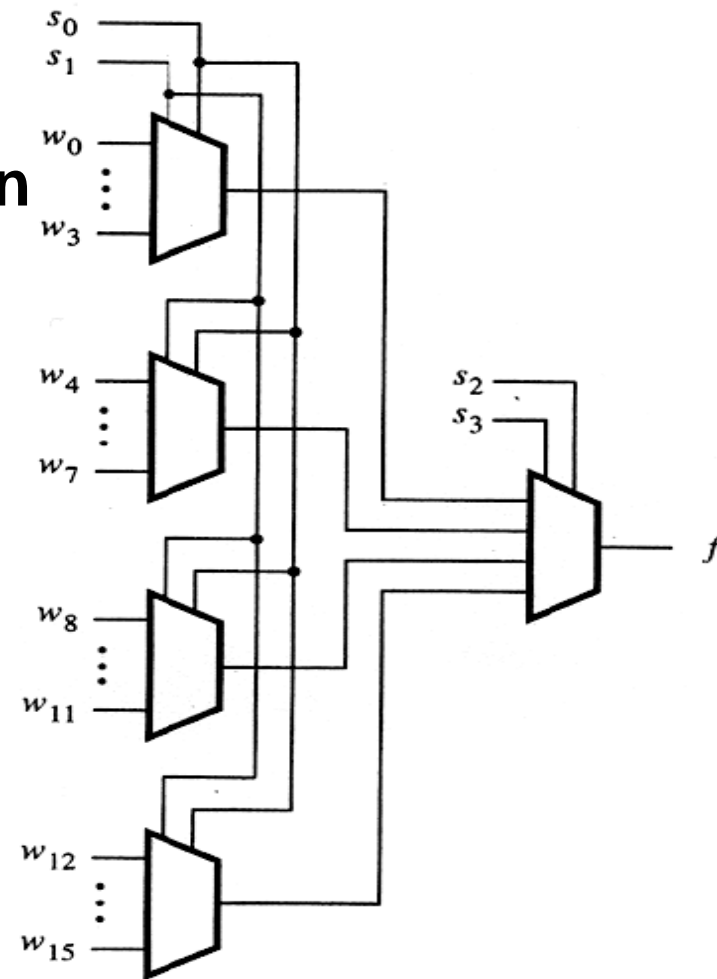- **16:1 Mux constructed from 4:1 Muxes.**
- **Expandable to 32:1 and 64:1 with additional 2:1 and/or 4:1 Muxes.**
- **With additional levels of propagation delay.**




Multiplexer Application

 - Crossbar Switch
- In general, n-inputs by n outputs
- Connectivity is any input to any output
- Important component of networking hardware
- The bigger, the faster, the better...



(a) A 2x2 crossbar switch

 

(b) Implementation using multiplexers


Combinational Design Using Multiplexers

- Input variables applied to Mux select lines “Steer” (constant) value of function to output
- Allows implementation of n-variable function with 2^n -to-1 multiplexer
- “Steer” derived function (a variable, its complement, the constant 1 or the constant 0) to the output
- Allows implementation of n-variable function with 2^{n-1} -to-1 multiplexer

Combinational Design Using Multiplexers


- Example 1: XOR Function
- Using a 4:1 Mux
- The modified Truth Table
 - Possibilities are x , x' , 0 , 1
- The 2-input XOR using a 2:1 Mux

w_1	w_2	f
0	0	0
0	1	1
1	0	1
1	1	0

 

w_1	w_2	f
0	0	0
0	1	1
1	0	1
1	1	0

w_1	f
0	w_2
1	\bar{w}_2

 

(a) Implementation using a 4-to-1 multiplexer

(b) Modified truth table


(c) Circuit

Combinational Design Using Multiplexers

- **Example 2 : Three input majority function**
- **Three input function with (2^{n-1} -to-1)**
- **4:1 Mux**

w_1	w_2	w_3	f		w_1	w_2	f
0	0	0	0	}	0	0	0
0	0	1	0		0	1	w_3
0	1	0	0	}	1	0	w_3
0	1	1	1		1	1	1
1	0	0	0	}			
1	0	1	1				
1	1	0	1	}			
1	1	1	1				

(a) Modified truth table

 

(b) Circuit

Combinational Design Using Multiplexers

■ Example 3 : Three input majority function with 2:1 Mux

□ Algebraic expansion

$$f(w_1, w_2, w_3) = (w_1 w_2 + w_1 w_3 + w_2 w_3)$$

$$f(w_1, w_2, w_3) = (w_1 w_2 + w_1 w_3 + w_2 w_3)(w_1' + w_1)$$

$$f = w_1'(w_1 w_2 + w_1 w_3 + w_2 w_3) + w_1(w_1 w_2 + w_1 w_3 + w_2 w_3)$$

... and from Shannon

$$f = w_1'(0w_2 + 0w_3 + w_2 w_3) + w_1(1w_2 + 1w_3 + w_2 w_3)$$

$$f = w_1'(w_2 w_3) + w_1(w_2 + w_3)$$

Combinational Design Using Multiplexers


■ Example 3: Three input majority function with 2:1 Mux

- Truth Table and circuit implementation

w_1	w_2	w_3	f
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

w_1	f
0	$w_2 w_3$
1	$w_2 + w_3$

(a) Truth table

 

(b) Circuit


Multiplexers and Buses

- Bus allows data transfers between multiple sources and single or multiple destinations over a shared path (wires).
- Bus includes multiple bits.
- Parallel data bus.
- Only one source on the bus at any time.
- Bus contention.

Multiplexers and Buses

 - Example below illustrates two, four-bit words (X and Y) multiplexed onto the Z bus.
- Register transfer operations.

$A' : Z \leftarrow X, A : Z \leftarrow Y$



Demultiplexer

- **Performs the reverse of a multiplexer.**
- **Accepts a single input and distributes it over several outputs.**
- **Select input code determines to which output the data input will be transmitted.**
- **It can be used as binary to decimal decoder with binary inputs applied at the select input lines and the output will be obtained on the corresponding line.**
- **It is useful in the design of multiple-output combinational circuit, because it needs minimum package count.**
- **It is available as 2-line-to-4-line, 3-line-to-8-line, and 4-line-to-16-line decoders.**
- **The output of most of these devices are active low, and it consists of a active-low enable/data input terminal.**
- **Decoder requires some gates in order to realize a boolean expression in the standard SOP form.**

Demultiplexers


- Serial to parallel conversion
 - Send a single data bit to a specific address
- A 1-to- 2^n demultiplexer is implemented using an n-to- 2^n decoder
 - The (value of) the data is applied via the enable input
- Valuable circuit in sequential circuits
 - Not so much in combinational circuits
- Also referred to as Dmux's

Demultiplexer Tree

- **Largest available decoders are 4-line-to-16-line decoders**
- **So to design a circuit for larger inputs, we make use of enable input terminals.**
- **E.g. 5-line-to-32-line decoder using two 4-line-to-16-line decoders**

Decoder

 - It has a set of inputs representing a binary number and gives only one output corresponding to the input number.
- It activates one output at a time depending upon the input binary number, all other outputs will be inactive.
- Figure shows the functional block diagram of a decoder having N inputs and K outputs. The possible combinations of N inputs will be $2^N = K$, so there will be K outputs.




Decoders


- 2-to-4 Decoder shown
 - 2-to- 2^n in general
 - Enable input allows construction of decoder tree and demultiplexer
 - Generates all minterms when enabled
 - Multiple output circuits
 - One hot decoding

En	w_1	w_0	y_0	y_1	y_2	y_3
1	0	0	1	0	0	0
1	0	1	0	1	0	0
1	1	0	0	0	1	0
1	1	1	0	0	0	1
0	x	x	0	0	0	0

(a) Truth table

 


(b) Graphical symbol

 

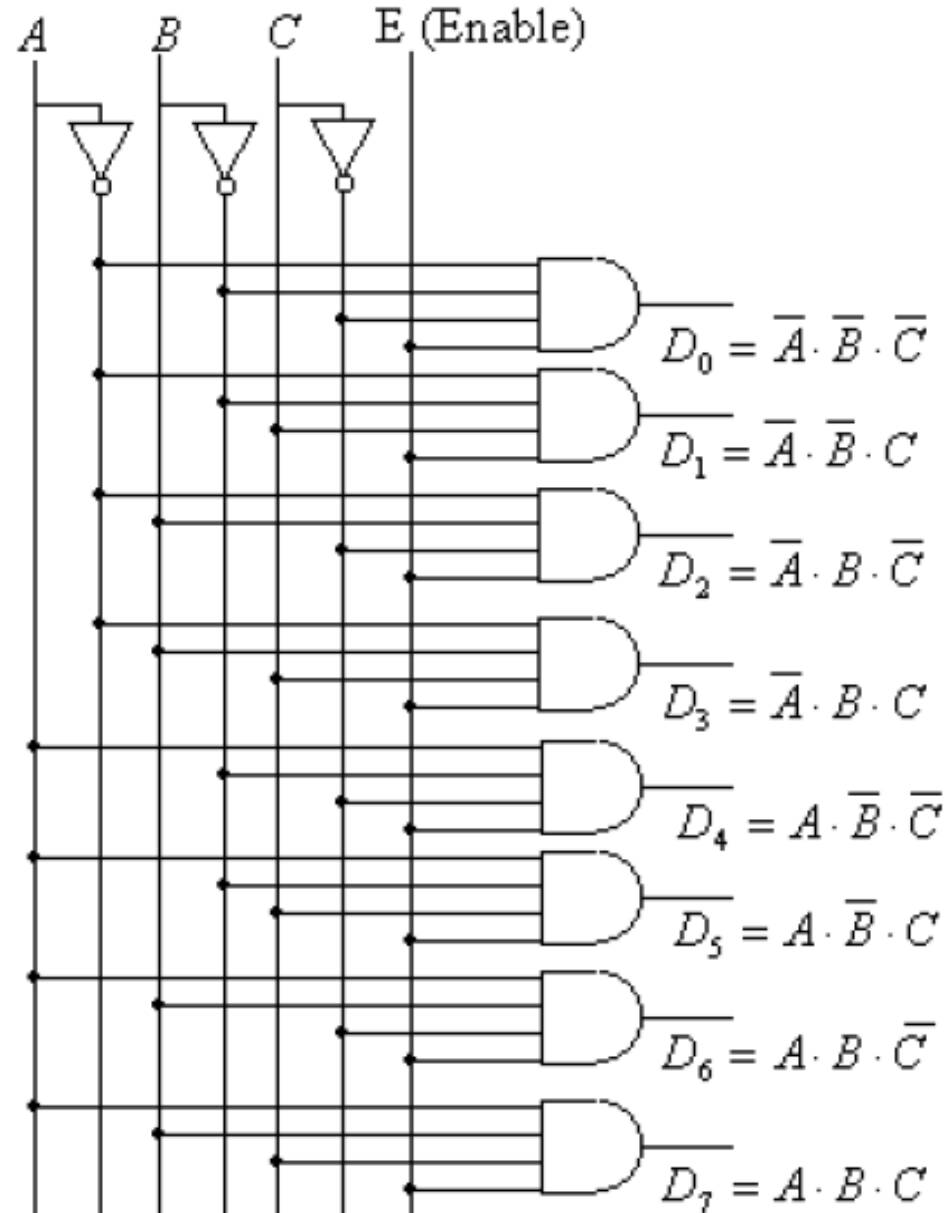(c) Logic circuit


3 to 8 line decoder

- It will have three input lines and $2^3 = 8$ output lines.
- When 3 bit binary number is fed to the input of the decoder, one output line corresponding to input binary is activated & all other output lines will be inactive.
- It is also called binary to octal decoder or converter.




Decoder Tree

 - One-bit expansion (3-to-8) by adding external decoding circuitry




Decoder Tree

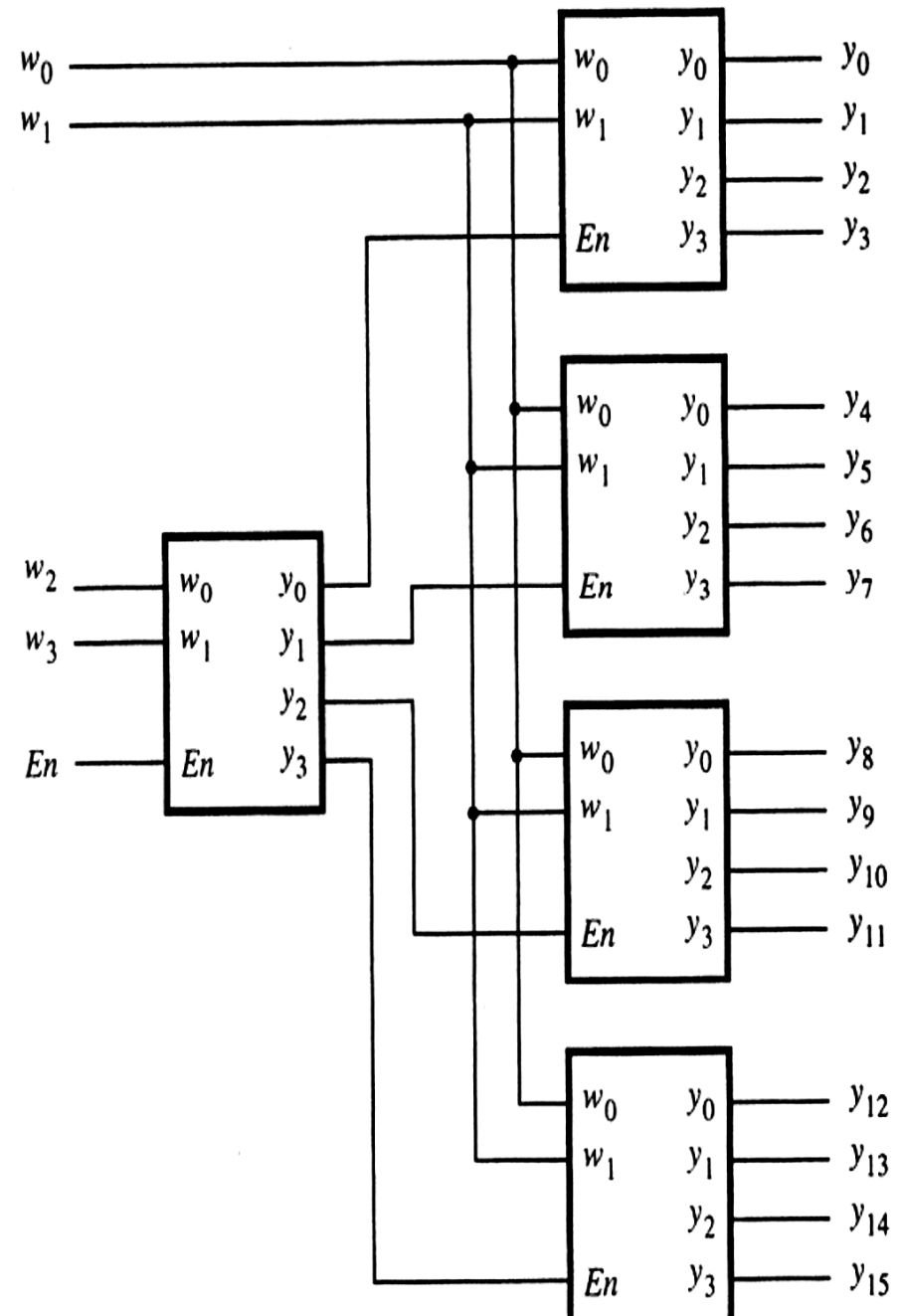- Two-bit expansion (4-to-16) by adding another 2-to-4 decoder



Decoder Applications

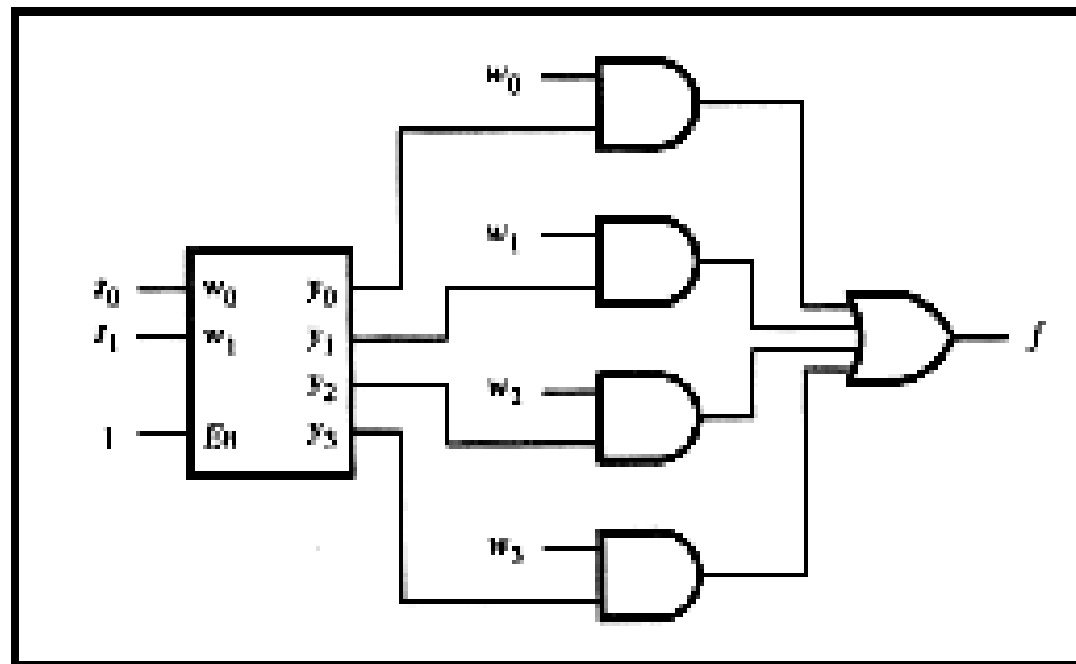
- Multiplexer from decoder
 - Recall "embedded decoder"



Decoder Applications

■ Multiple Output Circuits

□ Full Adder using 3 X 8 Decoder

 

$$\begin{aligned} \text{Sum} &= m_1 + m_2 + m_4 + m_7 \\ &= x'y'z + x'yz' + xy'z' + xyz \end{aligned}$$

$$\begin{aligned} \text{Carry} &= m_3 + m_5 + m_6 + m_7 \\ &= x'yz + xy'z + xy'z' + xyz \end{aligned}$$



Encoders

■ Binary Encoders

- "One hot" input, binary (or other code) representation output
- Reverse of decoder

w_3	w_2	w_1	w_0	y_1	y_0
0	0	0	1	0	0
0	0	1	0	0	1
0	1	0	0	1	0
1	0	0	0	1	1


(a) Truth table

  

(b) Circuit

Decoder Applications

■ Decoder Bus Control/Multiplexer

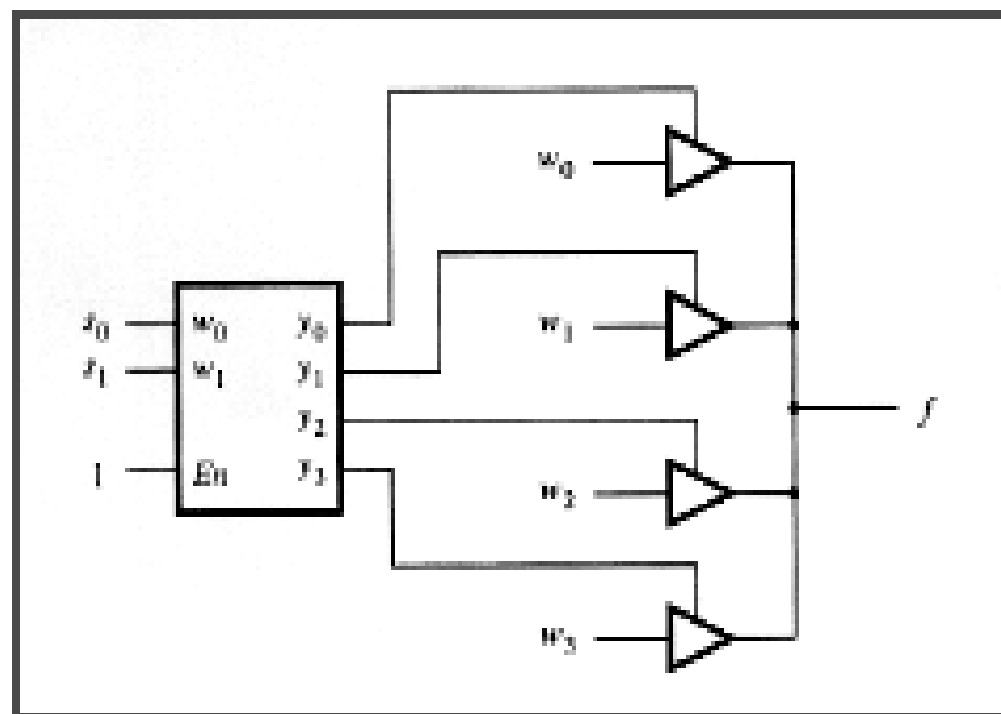

Combinational Logic Design

Decoder:

- It converts n-bit binary information at its input into a maximum of 2^n output lines.
- A decoder with enable input can function as a demux.


Inputs		Outputs			
A	B	D0	D1	D2	D3
0	0	1			
0	1		1		
1	0			1	
1	1				1

Encoder:

- It is just reverse of decoders.
- It has 2^n input lines and n output lines. The output lines generate the binary code corresponding to the input value.
- E.g. Decimal to BCD Encoder. IC available is (74147) decimal to BCD Priority Encoder.

Encoders

 - It is a combinational circuit which performs the reverse operation of decoder.
- It has a number of input lines, only one of which is activated at a time. It provides the N bit code at the output corresponding to activated input line.
- Figure shows the functional block diagram of an encoder having K inputs and N outputs.
- In the K input lines only one line will be high at a time.



■ Priority Encoders

- Used in prioritizing interrupts (or other events)


	Least significant				Binary encoding		
	w_3	w_2	w_1	w_0	y_1	y_0	z
Most significant	0	0	0	0	d	d	0
	0	0	0	1	0	0	1
	0	0	1	x	0	1	1
	0	1	x	x	1	0	1
	1	x	x	x	1	1	1
							Output valid

Priority Encoder

- In logic circuit for encoders, only one of the inputs is kept high at a time and output is obtained corresponding to the high input.
- But if two or more inputs are inadvertently activated at a time then undesirable results will be obtained.
- Priority encoder performs the same logic function as that of encoder with the additional facility of priority function.
- When two or more input lines are activated simultaneously. The priority function means that the encoder will provide the output corresponding to the highest order activated input line.

Magnitude Comparator

- It is also called as the magnitude digital (or binary) comparator.
- It compares and indicates if the binary number P is equal to or greater than or less than the other binary number Q.
- Let P_0 and Q_0 are the two bits to be compared. The result for the equality of these two bits may be given by XNOR gate.
- The XNOR gate gives an output as logic 1 if two bits are equal otherwise logic 0.
- The logic diagram for one bit comparator is shown in figure :

 

1-Bit Comparator

- It is used to compare two single bits and hence called a single bit comparator.
- It consists of two inputs each for two single bit numbers and three outputs to generate less than, equal to and greater than between two binary numbers.
- The truth table for a 1-bit comparator is given below:

A	B	$A < B$	$A = B$	$A > B$
0	0	0	1	0
0	1	1	0	0
1	0	0	0	1
1	1	0	1	0

- From the above truth table logical expressions for each output can be expressed as follows:
- $A > B$: AB'
- $A < B$: $A'B$
- $A = B$: $A'B' + AB$

1-Bit Comparator

➤ From the above expressions we can derive the following formula:

$$(A < B) + (A > B) = A'B + AB'$$

Taking complement both sides

$$(A < B) + (A > B)' = (A'B + AB')'$$

$$(A < B) + (A > B)' = (A'B)' (AB')'$$

$$(A < B) + (A > B)' = (A + B') (A' + B)$$


$$(A < B) + (A > B)' = (AA' + AB + A'B' + BB')$$

$$= (AB + A'B')$$

Thus,

$$(A < B) + (A > B)' = (A = B)$$

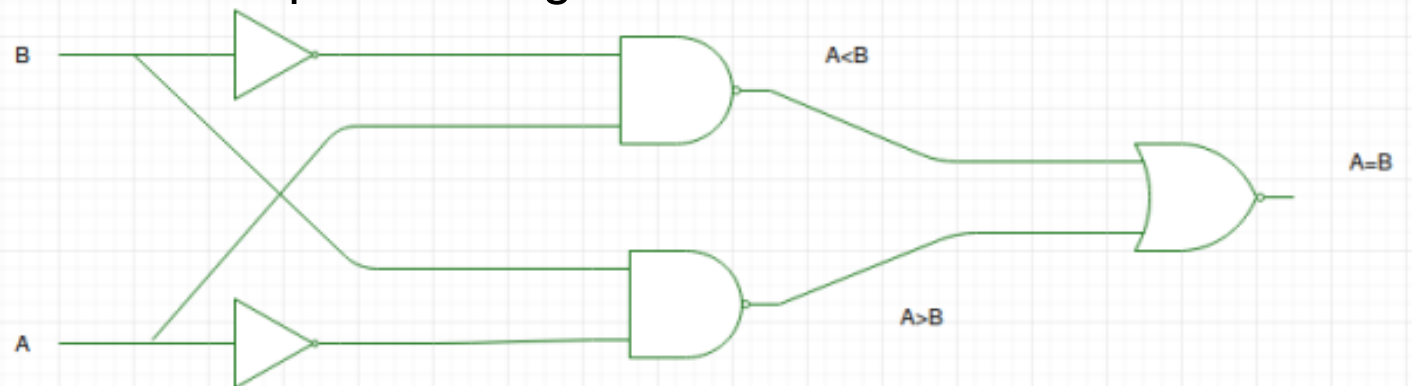By using these Boolean expressions, we can implement a logic circuit for this comparator as given below:



2-Bit Comparator

- It is used to compare two binary numbers each of two bits and hence called a 2-bit Magnitude comparator.
- It consists of four inputs and three outputs to generate less than, equal to and greater than between two binary numbers.
- The truth table for a 2-bit comparator is given below:

INPUT				OUTPUT		
A1	A0	B1	B0	A<B	A=B	A>B
0	0	0	0	0	1	0
0	0	0	1	1	0	0
0	0	1	0	1	0	0
0	0	1	1	1	0	0
0	1	0	0	0	0	1
0	1	0	1	0	1	0
0	1	1	0	1	0	0
0	1	1	1	1	0	0
1	0	0	0	0	0	1
1	0	0	1	0	0	1
1	0	1	0	0	1	0
1	0	1	1	1	0	0
1	1	0	0	0	0	1
1	1	0	1	0	0	1
1	1	1	0	0	0	1
1	1	1	1	0	1	0

2-Bit Comparator

➤ From the above truth table K-map for each output can be drawn as follows:

K-map for $A > B$

		B1B0	00	01	11	10
A1A0	00		0	0	0	0
	01		1	0	0	0
	11		1	1	0	1
	00		1	1	0	0

K-map for $A = B$

		B1B0	00	01	11	10
A1A0	00		1	0	0	0
	01		0	1	0	0
	11		0	0	1	0
	00		0	0	0	1


K-map for $A < B$

		B1B0	00	01	11	10
A1A0	00		0	1	1	1
	01		0	0	1	1
	11		0	0	0	0
	00		0	0	1	0



2-Bit Comparator

- From the above K-maps logical expressions for each output can be expressed as follows:
- **$A > B$: $A1B1' + A0B1'B0' + A1A0B0'$**
- **$A = B$: $A1'A0'B1'B0' + A1'A0B1'B0 + A1A0B1B0 + A1A0'B1B0'$**
: $A1'B1' (A0'B0' + A0B0) + A1B1 (A0B0 + A0'B0')$
: $(A0B0 + A0'B0') (A1B1 + A1'B1')$
: $(A0 \text{ Ex-Nor } B0) (A1 \text{ Ex-Nor } B1)$
- **$A < B$: $A1'B1 + A0'B1B0 + A1'A0'B0$**
- By using these Boolean expressions, we can implement a logic circuit for this comparator as given below:

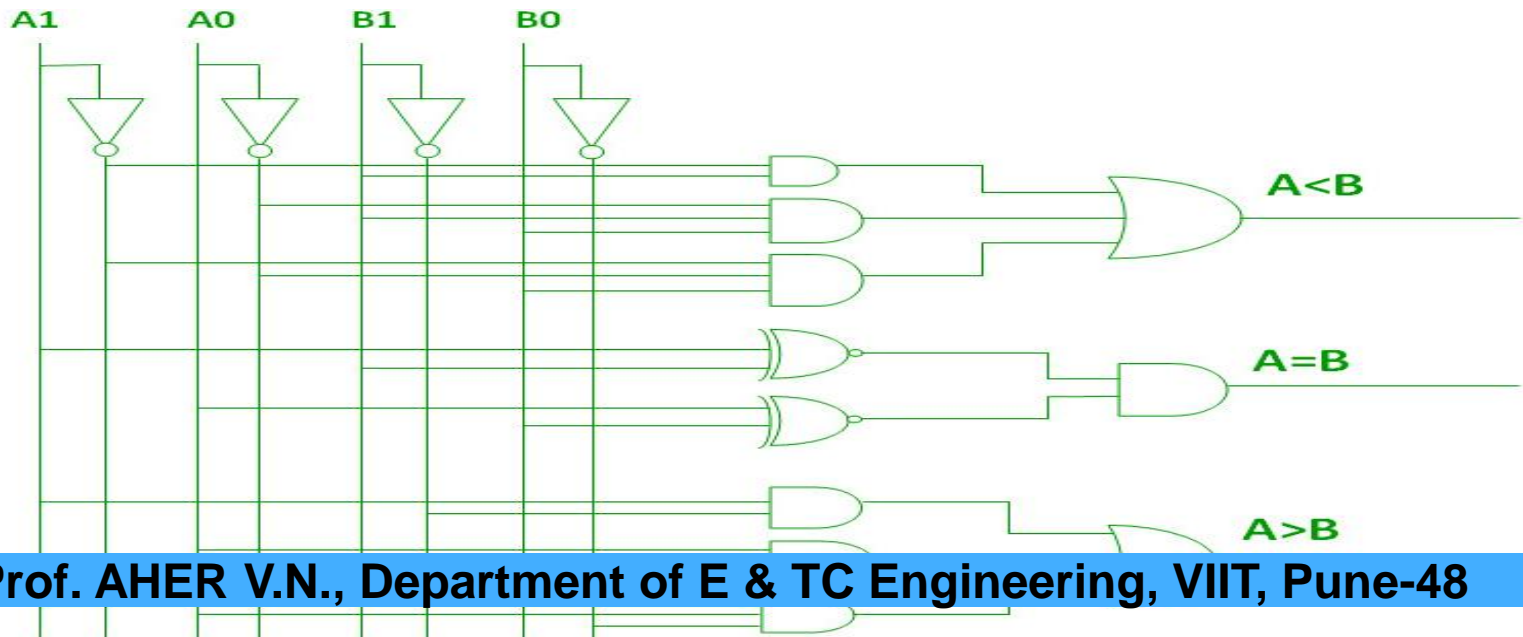

4-Bit Comparator

- It is used to compare two binary numbers each of four bits & hence called a 4-bit magnitude comparator.
- It consists of eight inputs each for two four bit numbers and three outputs to generate less than, equal to and greater than between two binary numbers.

In a 4-bit comparator the condition of $A > B$ can be possible in the following four cases:

- If $A_3 = 1$ and $B_3 = 0$
- If $A_3 = B_3$ and $A_2 = 1$ and $B_2 = 0$
- If $A_3 = B_3$, $A_2 = B_2$ and $A_1 = 1$ and $B_1 = 0$
- If $A_3 = B_3$, $A_2 = B_2$, $A_1 = B_1$ and $A_0 = 1$ and $B_0 = 0$

Similarly the condition for $A < B$ can be possible in the following four cases:

- If $A_3 = 0$ and $B_3 = 1$
- If $A_3 = B_3$ and $A_2 = 0$ and $B_2 = 1$
- If $A_3 = B_3$, $A_2 = B_2$ and $A_1 = 0$ and $B_1 = 1$
- If $A_3 = B_3$, $A_2 = B_2$, $A_1 = B_1$ and $A_0 = 0$ and $B_0 = 1$

The condition of $A = B$ is possible only when all the individual bits of one number exactly coincide with corresponding bits of another number.

4-Bit Comparator


➤ Truth table of 4-Bit Comparator :

COMPARING INPUTS				OUTPUT		
A3, B3	A2, B2	A1, B1	A0, B0	A > B	A < B	A = B
A3 > B3	X	X	X	H	L	L
A3 < B3	X	X	X	L	H	L
A3 = B3	A2 > B2	X	X	H	L	L
A3 = B3	A2 < B2	X	X	L	H	L
A3 = B3	A2 = B2	A1 > B1	X	H	L	L
A3 = B3	A2 = B2	A1 < B1	X	L	H	L
A3 = B3	A2 = B2	A1 = B1	A0 > B0	H	L	L
A3 = B3	A2 = B2	A1 = B1	A0 < B0	L	H	L
A3 = B3	A2 = B2	A1 = B1	A0 = B0	H	L	L
A3 = B3	A2 = B2	A1 = B1	A0 = B0	L	H	L
A3 = B3	A2 = B2	A1 = B1	A0 = B0	L	L	H
H = High Voltage Level, L = Low Voltage, Level, X = Don't Care						

A=B: (A3 Ex-Nor B3) (A2 Ex-Nor B2) (A1 Ex-Nor B1) (A0 Ex-Nor B0)


4-Bit Comparator

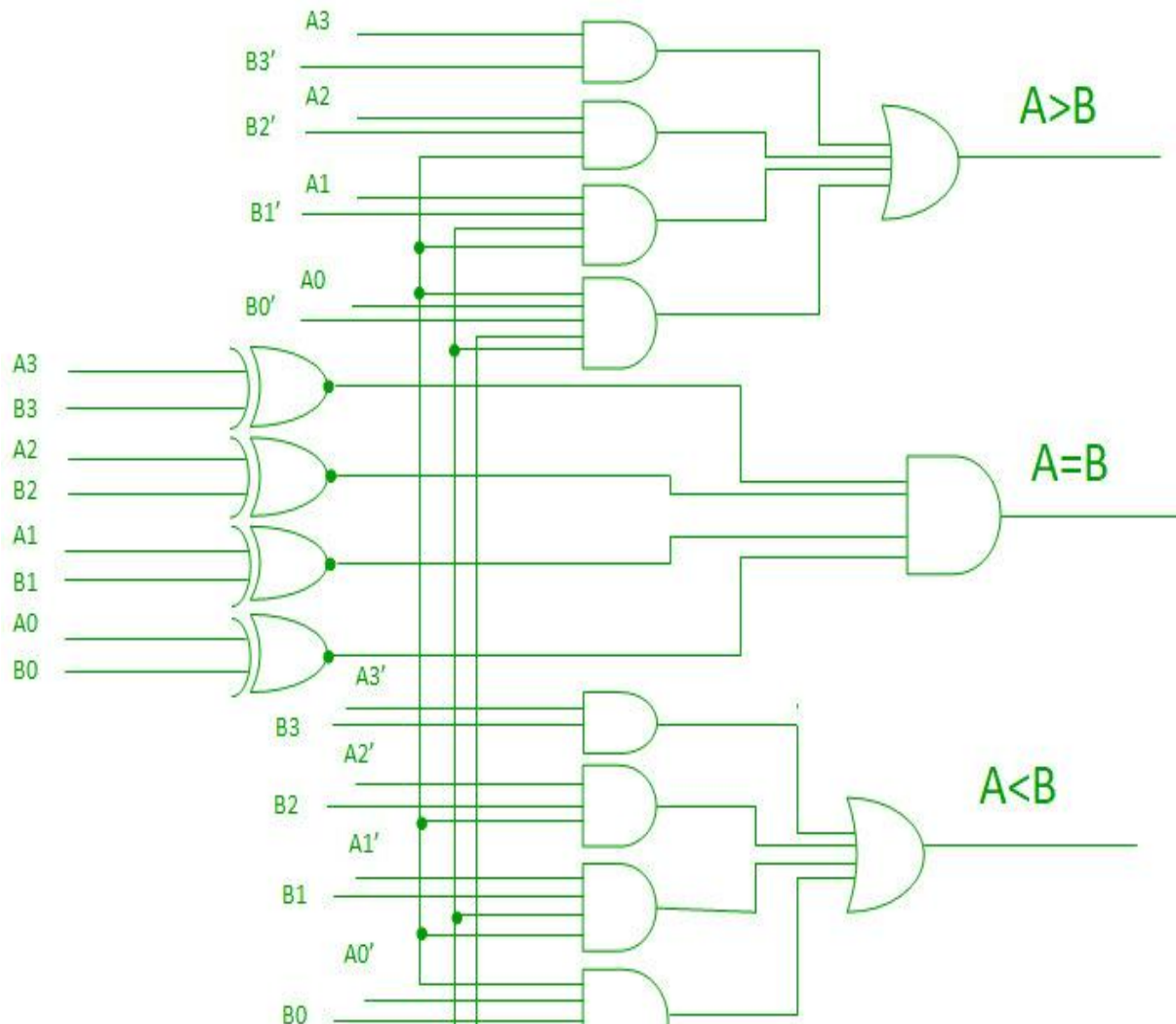- By using these Boolean expressions, we can implement a logic circuit for this comparator as given below:




4-Bit Comparator(IC-7485)

- Figure shows a 4-bit comparator.

 

Cascading Comparator

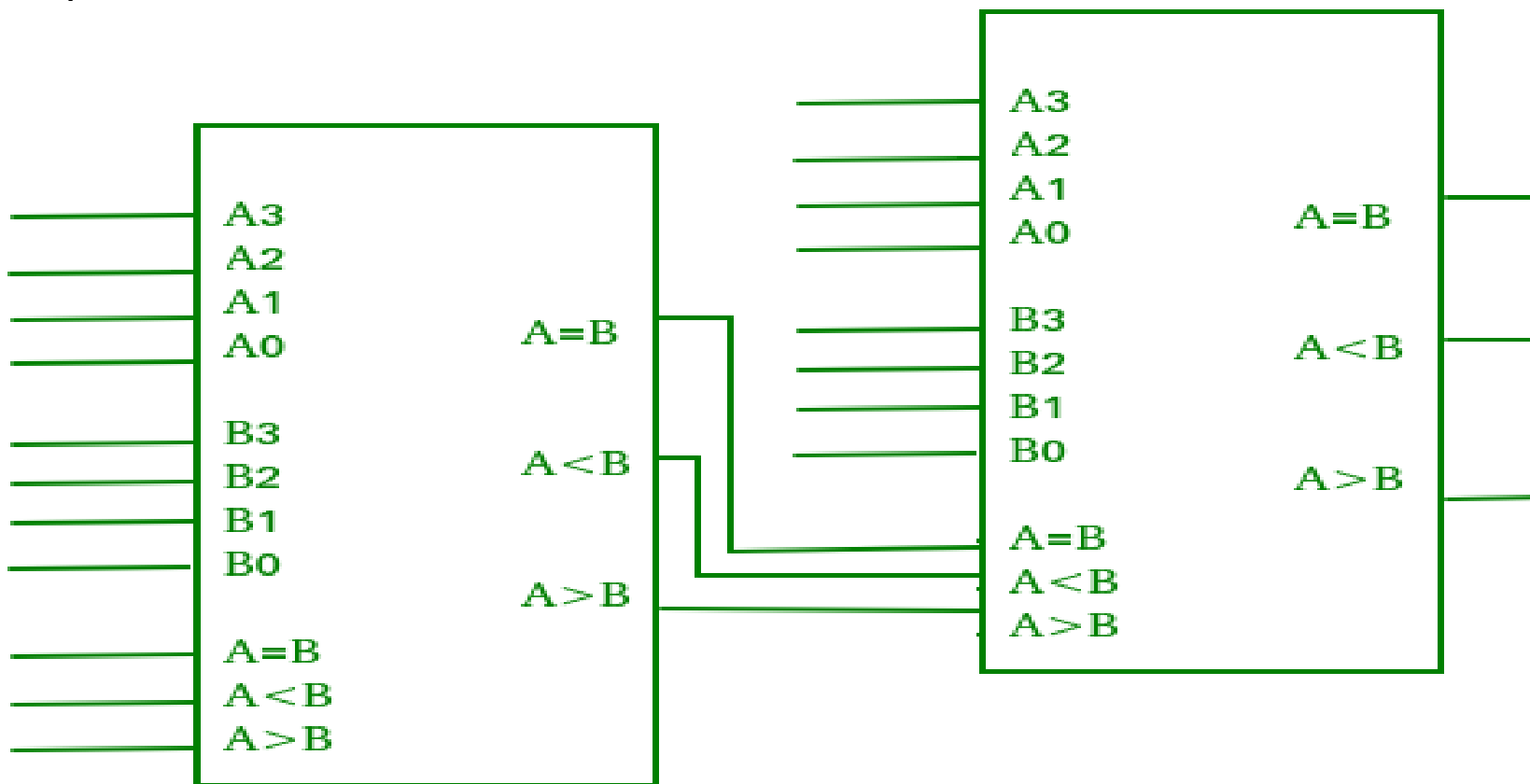- A comparator performing the comparison operation to more than four bits by cascading two or more 4-bit comparators is called cascading comparator.
- When two comparators are to be cascaded, the outputs of the lower-order comparator are connected to corresponding inputs of the higher-order comparator.



Applications of Comparators


- Comparators are used in central processing units (CPUs) and microcontrollers (MCUs).
- These are used in control applications in which the binary numbers representing physical variables such as temperature, position, etc. are compared with a reference value.
- Comparators are also used as process controllers and for Servo motor control.
- Used in password verification and biometric applications.

Parity Generator/Checker

- In the transmission of data in digital systems, error may occur due to change of data bit (0 by 1 or vice versa).
- This change may be due to component malfunctions or the electrical noise.
- This problem is removed by adding one additional bit in the data to be transmitted. This extra bit is known as parity bit.
- The parity bit detects the single error in the transmission.
- Parity is the number of 1's in the given data or word. If the number of 1's in the given data is even then parity is called as even parity; if on the other hand the number of 1's is odd then the parity is called as odd parity.
- The parity bit of the data or the word is generated by the parity generator.
- This parity generator gives output P (parity bit) as logic 1 if the number of 1's in the four bit input data is even; and P is logic 0 if the number of 1's in the four bit input data is odd.
- That is for even parity of the input data, output is 1 and for odd parity of the input data, output is 0.


Parity Generator/Checker

 - The logic diagram of the parity bit generator of four bit is shown in figure.




Parity Generator/Checker

- The parity bit P generated by the parity generator is sent along with the data and at the receiver end data as well as the parity bit is checked by the parity checker.
- The logic circuit for the parity checker is the same as that of the parity generator with the only difference that in the parity checker the terminal P' is not grounded, but the parity bit received at the receiver end is connected to the point P' .
- So at the receiver the received data and the parity bit form the five bit data which is always having the odd parity.
- It is clear from the fact that if the data A, B, C and D is odd (even) then parity bit is 0 (1), and therefore the received data and the parity bit is always is odd.

 

Parity Generator/Checker(IC-74180)

 - Parity generator/checker is available in the form of IC.
- Figure shows the block diagram of 8 bit parity generator/checker IC 74180 and its truth table.
- It can be used to check for even or odd parity on a 9 – bit code (8 – bit data and one parity bit).
- It can also be used to generate a 9 – bit even or odd parity code.



Parity of 8 bit data	Inputs		Outputs	
	Even	Odd	Σ_{even}	Σ_{Odd}
Even	1	0	1	0
Odd	1	0	0	1
Even	0	1	0	1
Odd	0	1	1	0
ϕ	1	1	0	0
ϕ	0	0	1	1

Review of Unit-1 & 2

Representation of Logical Functions

Simplification of Logical Functions using K-map:

Prime Implicant:

- It is a group of minterms that cannot be combined with any other minterm or groups.

Essential Prime Implicant:

- It is a prime – implicant in which one or more minterms are unique i.e. it contains at least one minterm which is not contained in any other prime- implicant.

Standard Representation for Logical Functions: The logic functions can be expressed in the following forms:

1. **Sum of Product (SOP):** For minterm 1 → normal variable (A) & 0 is complement var. (\bar{A})
2. **Product of Sum (POS):** For maxterm 1 → complement Var. (\bar{A}) & 0 is normal var. (A)

Standard or Canonical Form:

- If each term in SOP and POS forms contains all the literals then these are known as Standard (or Canonical) SOP and POS respectively. Each term in standard SOP is minterm & in Standard POS is maxterm.

Minimization of Logical Functions:

1. **Minimization of SOP Form:** If the expression is simplified to a stage beyond which it cannot be further simplified, it will require minimum number of gates with minimum no. of inputs to the gates. Such an expression is referred to as the minimized expression.
2. **Minimization of POS Form:**

Representation of Logical Functions

Don't Care Conditions:

- In some cases certain combinations of input variables do not occur. Also, for some functions the outputs corresponding to certain combinations of input variables do not matter. These conditions are called as don't care condition.

Combinational Logic Design

Combinational Logic Design Using MSI Circuits:

- The circuits which we have studied involves simplification & realization using gates. Thus using these methods, complex functions have been integrated and available in IC form.

Multiplexer:

- It is a special combinational circuit that is one of the most widely used.
- Multiplexer or data selector is a logic circuit that gates one out of several inputs to a single output.
- The selected input is controlled by a set of select inputs.
- Depending on select inputs, one out of n data sources is selected and transmitted to a single output channel.
- A Strobe or enable input (G) is incorporated which helps in cascading and it is generally active - low.

Combinational Logic Design

Advantages of using Mux:

1. Simplification of logic expression is not required.
2. It minimizes the IC package count.
3. Logic design is simplified.

Design Procedure:

1. Identify the decimal number corresponding to each minterm in the expression. The input lines corresponding to these numbers are connected to logic 1 level.
2. All the other inputs are connected to 0.
3. The inputs are to be applied to select inputs.

Combinational Logic Design

E.g. 1. Implement the expression using a mux,

- $F(A,B,C,D) = \sum m(0,2,3,6,8,9,12,14)$ Ans. Since 4 var. hence mux with 4 select inputs required.

E.g. 2. Realize the logic function of the truth table using 8:1 multiplexer using LSB method.

A	B	C	D	Y
0	0	0	0	0
0	0	0	1	0
0	0	1	0	1
0	0	1	1	0
0	1	0	0	1
0	1	0	1	0
0	1	1	0	1
0	1	1	1	1
1	0	0	0	0
1	0	0	1	1
1	0	1	0	1
1	0	1	1	1
1	1	0	0	1
1	1	0	1	0
1	1	1	0	0
1	1	1	1	1

Combinational Logic Design

Cascading of Multiplexer (Multiplexer Tree):

- Multiplexers with more number of inputs can be obtained by cascading two or more multiplexers with less number of inputs. This is called as multiplexer tree.
- E.g. The cascading of two 4:1 multiplexer results in 8:1 multiplexer.
- The select lines s_1 & s_0 of both 4:1 multiplexers are connected in parallel whereas a third select input s_2 is used for enabling one multiplexer at a time.

Demultiplexer:

- The number of output lines n and select lines m where $n=2^m$.
- It can be used as binary-to-decimal decoder.
- Binary input is given at select input lines & the output is obtained on corresponding line. The data input line is to be connected to logic 1.
- The device is also called as 2-line-to-4-line, 3-line-to-8-line & 4-line-to-16-line decoder.
- It requires some gates to realize boolean expressions in the standard SOP form.

Combinational Logic Design

E.g. Implement the following multi-output combinational logic circuit using a 4-to-16-line decoder.

$$f1 = \sum m(1, 2, 4, 7, 8, 11, 12, 13)$$

$$f2 = \sum m(2, 3, 9, 11)$$

$$f3 = \sum m(10, 12, 13, 14)$$

$$f4 = \sum m(2, 4, 8)$$

Decoder:

- It converts n-bit binary information at its input into a maximum of 2^n output lines.
- A decoder with enable input can function as a demux.



Inputs		Outputs			
A	B	D0	D1	D2	D3
0	0	1			
0	1		1		
1	0			1	
1	1				1

Combinational Logic Design

Encoder:

- It is just reverse of decoders.
- It has 2^n input lines and n output lines. The output lines generate the binary code corresponding to the input value
- E.g. Decimal to BCD Encoder. IC available is (74147) decimal to BCD Priority Encoder.

  ■ BCD to 7-Segment Display Code Converter



w_3	w_2	w_1	w_0	a	b	c	d	e	f	g
0	0	0	0	1	1	1	1	1	1	0
0	0	0	1	0	1	1	0	0	0	0
0	0	1	0	1	1	0	1	1	0	1
0	0	1	1	1	1	1	1	0	0	1
0	1	0	0	0	1	1	0	0	1	1
0	1	0	1	1	0	1	1	0	1	1
0	1	1	0	1	0	1	1	1	1	1
0	1	1	1	1	1	1	0	0	0	0
1	0	0	0	1	1	1	1	1	1	1
1	0	0	1	1	1	1	1	0	1	1

(a) Code converter

(b) 7-segment display

(c) Truth table

End of Unit-2